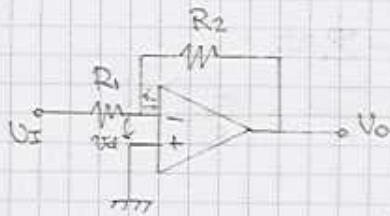


# AMPLIFICATORI OPERAZIONALI

## INVERTENTE




CONDIZIONE:  $V_{Omin} \frac{R_1}{R_1+R_2} \leq V_{in} \leq V_{Omax} \frac{R_1}{R_1+R_2}$  (RAD)

CASO IDEALE:  $V_O = -\frac{R_2}{R_1} V_I = -A_v V_I \rightarrow f(s) = -\frac{R_2(s)}{R_1(s)}$


CASO REALE:  $V_O = -\frac{R_2}{R_1} \frac{1}{1 + \frac{1}{A_v}} \left(1 + \frac{R_2}{R_1}\right) V_I$

### ALIMENTI SATURAZIONE

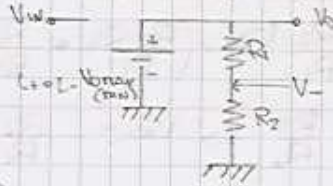


$V_{Omax} = -L \frac{R_1}{R_2}$  ;  $V_{Omin} = -L \frac{R_1}{R_2}$

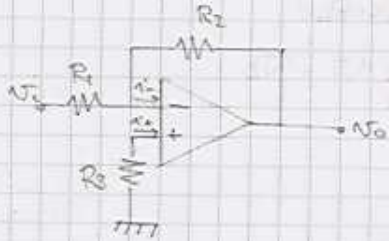$V_O = -\frac{R_2}{R_1} V_I$  (e come se  $R_3 = 0$ )




$V_O = -\frac{R_2}{R_1} V_I - \frac{R_2}{R_3} \frac{R_1+R_2}{R_1}$  ;  
 $V_I = V_{I+} = V_{I-} \Rightarrow V_O = 0 \Rightarrow R_3 = \frac{R_1 R_2}{R_1+R_2} = R_1 || R_2$  ;  $V_O = -\frac{R_2}{R_1} V_I$

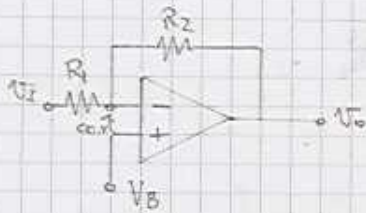

$V_O = -\frac{R_2}{R_1} V_I + V_B \frac{R_1+R_2}{R_1}$

## NON INVERTENTE

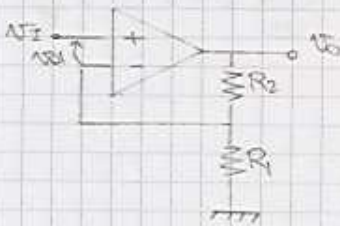

CASO IDEALE:  $V_O = \frac{R_1+R_2}{R_1} V_I$  ;  $A_v = \frac{R_1+R_2}{R_1}$

CASO REALE:  $V_O = \frac{A_v}{1 + \frac{1}{A_v} \left(\frac{R_1}{R_1+R_2}\right)} V_I$

## CONVERTITORE CORRENTE - TENSIONE



CASO IDEALE:  $I_i = 0$  ;  $V_O = -I_i R_2$

CASO REALE:  $I_i \neq 0$  ;  $V_O = -R_2 (I_i - I_i')$


$I_i' = \frac{-V_O + I_i}{R_2}$

## FOLLOWER



$V_O = V_I$

## SOMMATTORE

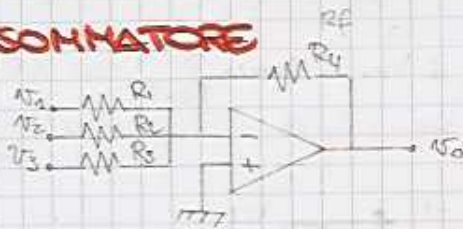


$$V_o = \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) (-R_f)$$

$$\approx R_1 = R_2 = R_3 = R_f \quad V_o = -\sum V_i$$

$$\approx V_i = 0 \Rightarrow R_i = 0 \quad \sum \frac{V_{i, \text{max}}}{R_i} = \frac{V_{\text{max}}}{R_f}$$
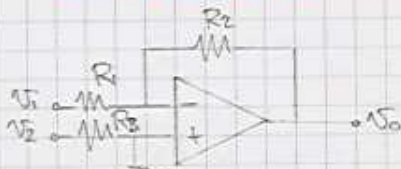
## SOTRAENTE (AMPLIFICATORE DIFFERENZIALE)



$$V_o = -\frac{R_2}{R_1} V_1 + \left( \frac{R_1 + R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} \right) V_2$$

$$\approx \frac{R_1}{R_2} = \frac{R_3}{R_4} \rightarrow V_o = -\frac{R_2}{R_1} V_1 + V_2$$

$$A_D = \frac{R_4}{R_3} \left( 1 + \frac{R_2}{R_1} \right)$$

$$V_o = V_1 \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) = V_1 \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_3}{R_4}}$$

## INTEGRATORE INVERTENTE



$$V_o = -\frac{1}{RC} \int V_i dt$$


$$V_o(t) = -\frac{1}{RC} \int V_i(t) dt + V_o$$

SAT



$$-C \frac{dV_o}{dt} = I_o = I_R = \frac{V_i}{R}$$


## DERIVATORE INVERTENTE

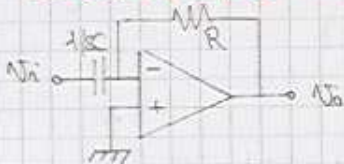

$$V_o = -RC \frac{dV_i}{dt}$$


$$V_o(f) = -RC \frac{dV_i}{dt}$$

## INTEGRATORE DI MILLER

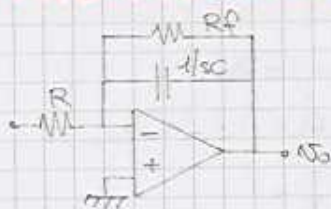

$$V_o = -\frac{R_f}{R} \frac{1}{1 + sR_f C} V_i$$
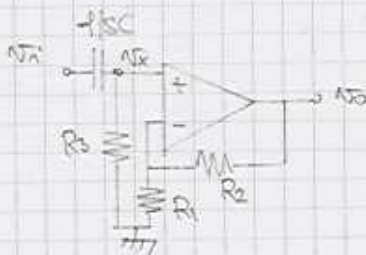
$$A_{DC} = -\frac{R_f}{R} \quad \omega_{-3dB} = \frac{1}{R_f C}$$



$$V_o = \frac{R_1 + R_2}{R} V_x = \frac{R_1 + R_2}{R} \frac{sCR_3}{1 + sCR_3} V_i$$

$$V_x = \frac{sCR_3}{1 + sCR_3} V_i$$